


# Alternating voltage and current

So far  $V = \text{constant}$  (e.g. battery)

This class  $V(t) = V_m \sin(\omega t + \phi)$

$t$  → time  
 $V_m$  → amplitude  
 $\omega$  → frequency  
 $\phi$  → phase

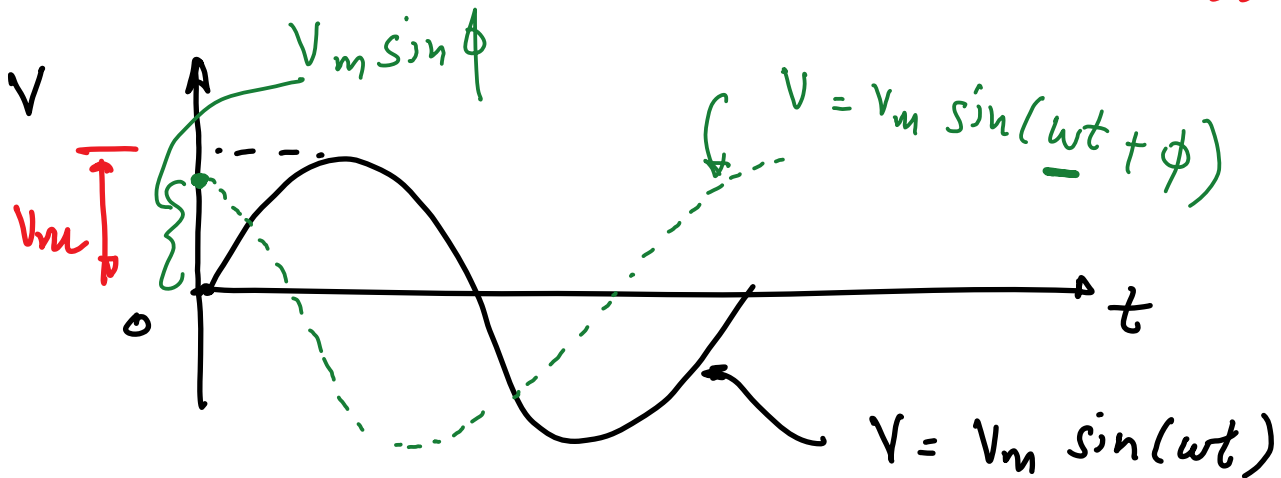$\phi > 0$  leading  
 $\phi < 0$  lagging




$$\omega \rightarrow \frac{1}{s} = s^{-1}$$

$$f = \frac{\omega}{2\pi}$$

Complex numbers e.g.  $2 + 3j$

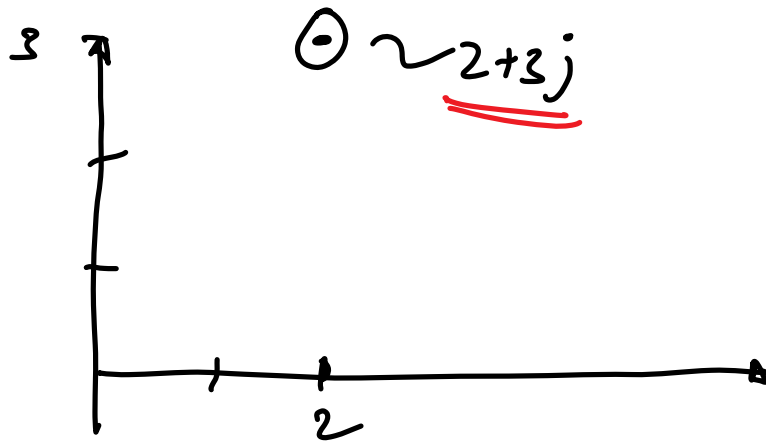$\uparrow$  real (x-axis)  
 $\nwarrow = \sqrt{-1}$  complex (y-axis)



$$\underline{e^{j(\omega t + \phi)}} = \underline{\cos(\omega t + \phi)} + j \underline{\sin(\omega t + \phi)}$$

$$\begin{aligned}
 \underline{V} &= V_m e^{j(\omega t + \phi)} = V_m [\cos(\omega t + \phi) + j \sin(\omega t + \phi)] \\
 &= V_m \angle \phi
 \end{aligned}$$

rectangular form

polar form

$$V = V_x + j V_y$$

$$V_m = \sqrt{V_x^2 + V_y^2}$$

$$\phi = \tan^{-1} \left( \frac{V_y}{V_x} \right)$$

Idea:

$$\frac{V}{I} = z \text{ (impedance, can be complex numbers)}$$

└──────────┘

$$\sim \frac{V}{I} = R$$

---

Resistor

$$V = RI$$

↓

$$V = z_R I$$

$$(z_R = R)$$

---

Inductor

$$V = L \frac{dI}{dt} \quad \rightsquigarrow \quad V = z_L I$$

$$\text{let } I = I_m e^{j(\omega t + \phi)}$$

$$\frac{dI}{dt} = I_m e^{j(\omega t + \phi)} \frac{d}{dt} [j(\omega t + \phi)]$$

$$= I_m e^{j(\omega t + \phi)} (j\omega)$$

---

$$V = L \underbrace{I_m e^{j(\omega t + \phi)}}_I (j\omega)$$


$$V = (j\omega L) I$$

$$= z_L I$$


$$z_L = j\omega L$$

If  $\omega = 0$  DC source ;  $z_L = 0$

short circuit  
(0 resistance)

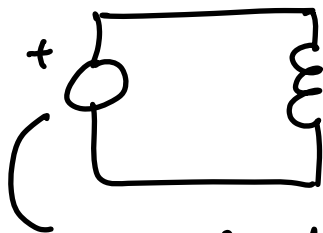

$V = \text{constant } (\omega = 0)$

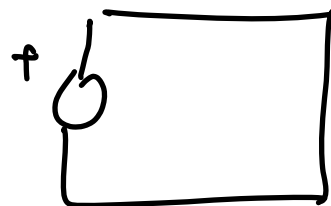

short circuit  
0 resistance

# Capacitor

$$q = CV \quad \rightsquigarrow \quad V = \frac{1}{C} I$$

$$\frac{dq}{dt} = C \frac{dV}{dt}$$

$$I = C \frac{dV}{dt}$$

$$V = V_m e^{j(\omega t + \phi)}$$

$$\frac{dV}{dt} = V_m e^{j(\omega t + \phi)} (j\omega)$$

$$I = C \underbrace{V_m e^{j(\omega t + \phi)}}_V (j\omega)$$

$$I = j\omega C V$$

$$\underline{I} = j\omega C \underline{V}$$



$$V = \frac{\underline{I}}{j\omega C} = \frac{j}{j^2} \frac{\underline{I}}{\omega C}$$

$$j = \sqrt{-1} \Rightarrow j^2 = -1$$

$$V = -\frac{j}{\omega C} \underline{I} \approx Z_C \underline{I}$$


$$Z_C = \frac{-j}{\omega C}$$

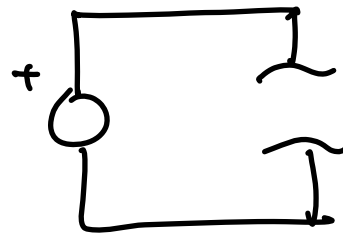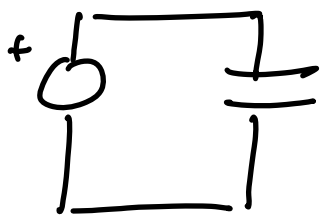For a DC source  $\omega = 0$   $Z_C = \infty$




open  
circuit  
 $I \approx 0$

Example

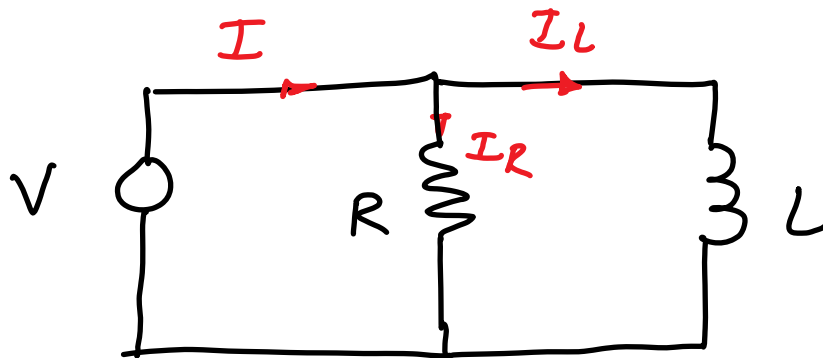


$V = \text{AC source}$

Compute  $I, I_L, I_R$ .

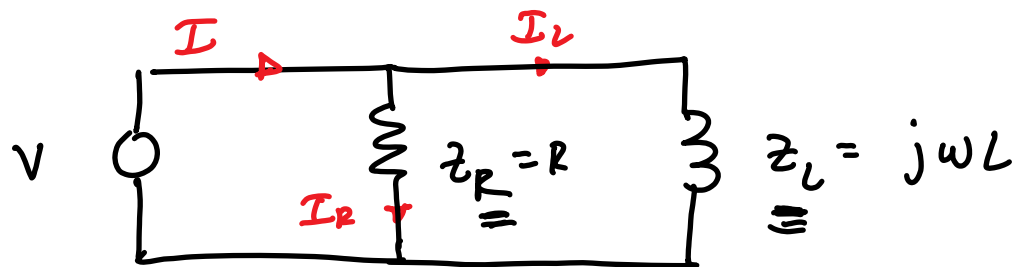


$$z = \frac{z_R z_L}{z_R + z_L} \quad (z_R \text{ \& \ } z_L \text{ are in parallel})$$
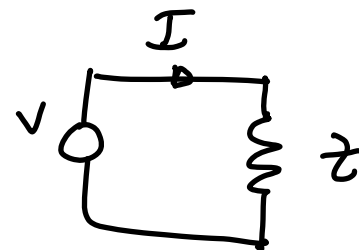
$$I = \frac{V}{z} = \frac{V (z_R + z_L)}{z_R z_L}$$



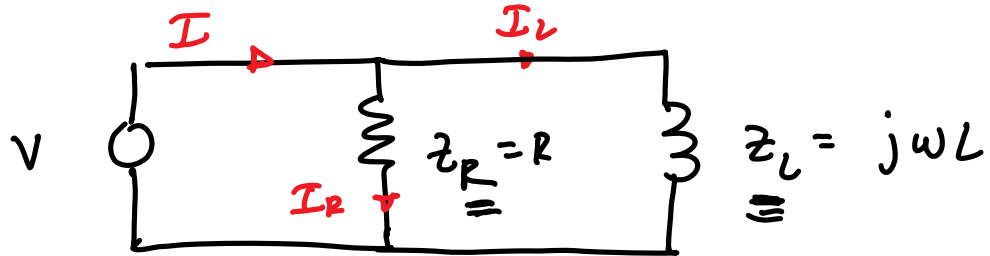
$$I = \frac{V (R + j\omega L)}{j\omega L R}$$



$I \checkmark$

$$I_1 = \frac{R_2}{R_1 + R_2} I$$

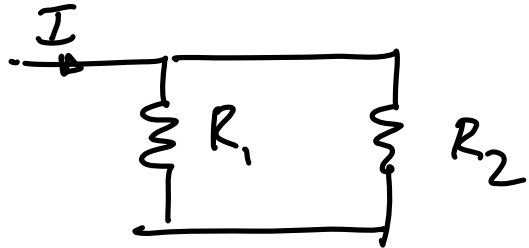

current divider

$$I_2 = \frac{R_1}{R_1 + R_2} I$$

$$I_R = \frac{z_L}{z_R + z_L} I = \frac{z_L}{z_R + z_L} \frac{V}{z_R + z_L}$$

$$I_R = \frac{V}{z_R} = \frac{V}{R}$$

$$I_L = \frac{z_R}{z_R + z_L} I = \frac{z_R}{z_R + z_L} \frac{V}{z_R + z_L}$$

$$I_L = \frac{V}{z_L} = \frac{V}{j\omega L}$$